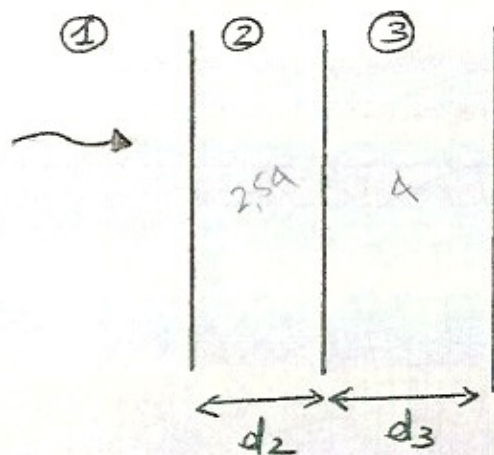


EXERCISE (Reflection on a multilayered dielectric)

Calculate the power reflection and transmission for the structure shown in the picture




$$\epsilon_{r1} = 1 \quad \epsilon_{r2} = 2.54 \quad \epsilon_{r3} = 4$$

$$d_2 = 2 \text{ mm} \quad d_3 = 3 \text{ mm}$$

$$f = 10 \text{ GHz} \quad (\lambda_0 = 3 \text{ cm})$$

$$\lambda = \frac{c}{f} = 3 \text{ cm}$$

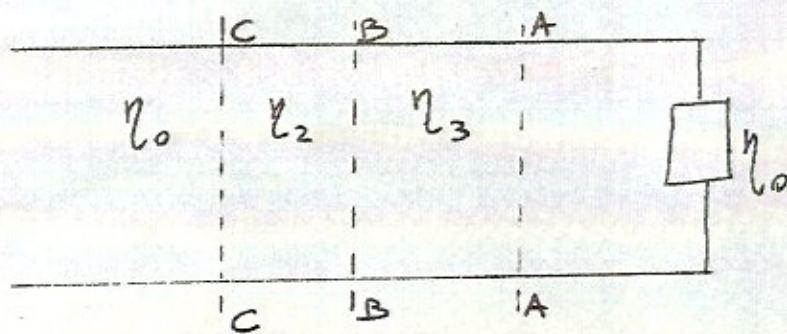Let's consider the equivalent transmission line



$$\eta_0 = 377 \Omega$$

$$\eta_2 = \frac{\eta_0}{\sqrt{\epsilon_{r2}}} = 236,5 \Omega$$

$$\eta_3 = \frac{\eta_0}{\sqrt{\epsilon_{r3}}} = 188,5 \Omega$$

To calculate the reflection coefficient Γ_{cc} , we start from the load section A and move back toward the "generator"

Each section of the line has the following "electrical" length (geometric length normalized to λ)

$$\frac{d_2}{\lambda_2} = \frac{2 \cdot 10^{-3} \sqrt{2,54}}{3 \cdot 10^{-2}} = 0,106$$

$$\frac{d_3}{\lambda_3} = \frac{3 \cdot 10^{-3} \sqrt{4}}{3 \cdot 10^{-2}} = 0,2$$

The normalized impedance at section A is


$$\bar{\eta}_{AA} = \frac{\eta_A}{\eta_3} = 2$$

The normalized impedance at section B is obtained by rotating point $\bar{\eta}_{AA}$ around the origin of the Smith Chart for a length d_3/λ_3

$$\bar{\eta}_{BB}^{(3)} = 0,53 - j0,24 \quad (\text{normalized to } \eta_3)$$

$$\eta_{BB} = \bar{\eta}_{BB} \eta_3 = 100 - j45 \Omega$$

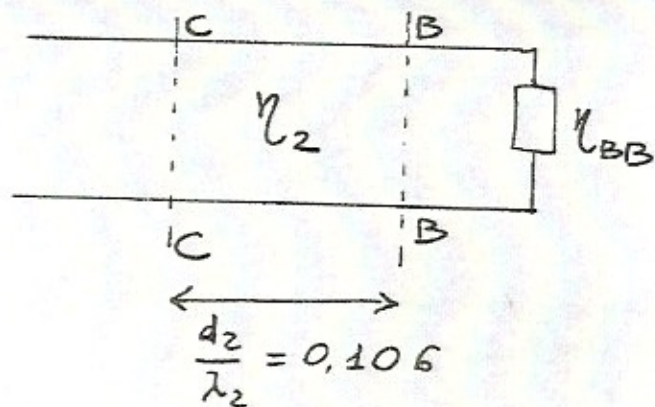The circuit is now equivalent to the one shown here below



Let's normalize η_{BB} to $\eta_2 = 236,5 \Omega$

$$\bar{\eta}_{BB}^{(2)} = \frac{\eta_{BB}}{\eta_2} = 0,42 - j0,19 \quad (\text{normalized to } \eta_2)$$

To move from section B to section C, rotate the point $\bar{\eta}_{BB}$ around the origin of the Smith Chart for a length

$$d_2/\lambda_2 = 0,106$$

$$\bar{\eta}_{cc} = 0,485 + j0,38 \quad (\text{normalized to } \eta_2)$$

$$\eta_{cc}^{(2)} = \bar{\eta}_{cc} \eta_2 = 114,2 + j90 \quad \Omega$$

The reflection coefficient at section C is simply given by

$$\Gamma_C = \frac{\eta_{cc} - \eta_0}{\eta_{cc} + \eta_0} = -0,484 + j0,22 = 0,555 e^{j2,63}$$

$$\angle \Gamma_C = 150,2^\circ$$

Note Γ_C can be also evaluate by normalizing η_{cc} to η_0 (see Smith Chart) and measuring $|\Gamma_C|$ and $\angle \Gamma_C$ directly onto the chart

$$\eta_{cc}^{(0)} = 0,3 + j0,24$$

The reflected power $\frac{P_R}{P_{in}} = |\Gamma|^2 = 0,305 \quad (30,5\%)$

The transmitted power (lossless medium) is


$$\frac{P_T}{P_{in}} = 1 - |\Gamma|^2 = 0,695 \quad (69,5\%)$$

Smith Chart


4 Mc
 150°

$\frac{d_s}{\lambda_g} = 0.106$

$\frac{d_r}{\lambda_g} = 0.2$

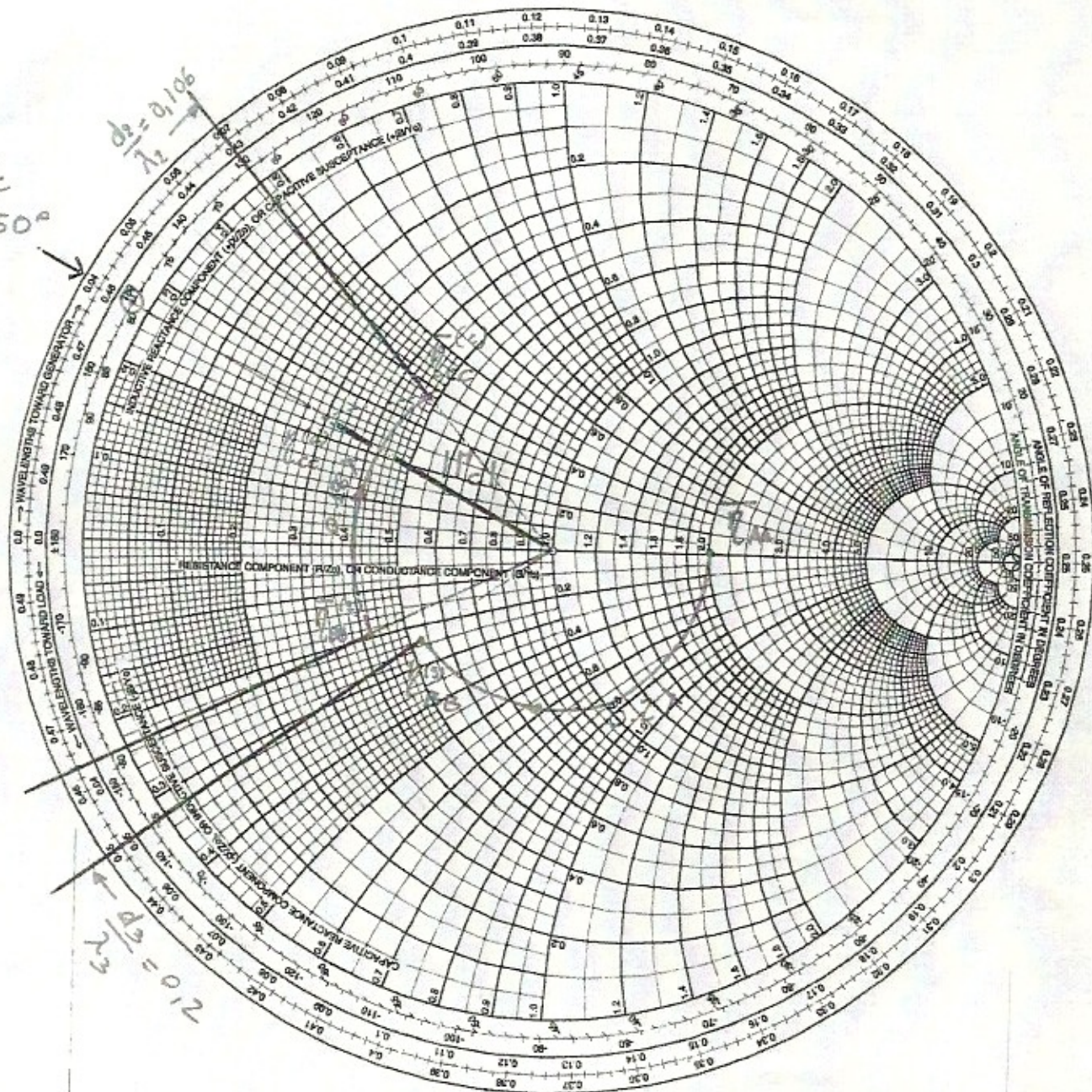


RADIALLY SCALED PARAMETERS

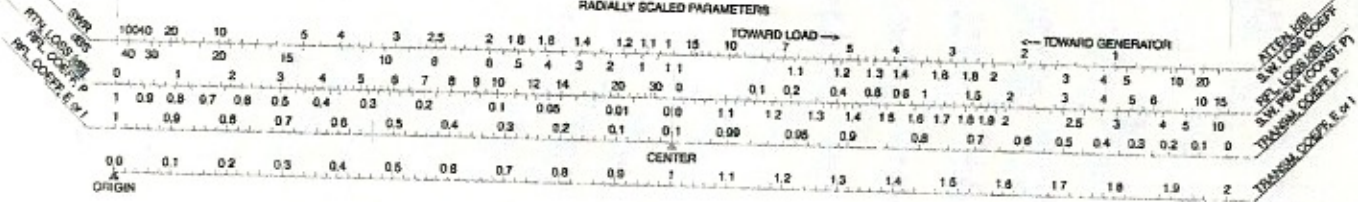

AFTER LOSS
 SWR LOSS COEFF
 REF LOSS COEFF
 TRANSM LOSS COEFF (P)
 TRANSM LOSS COEFF (V)

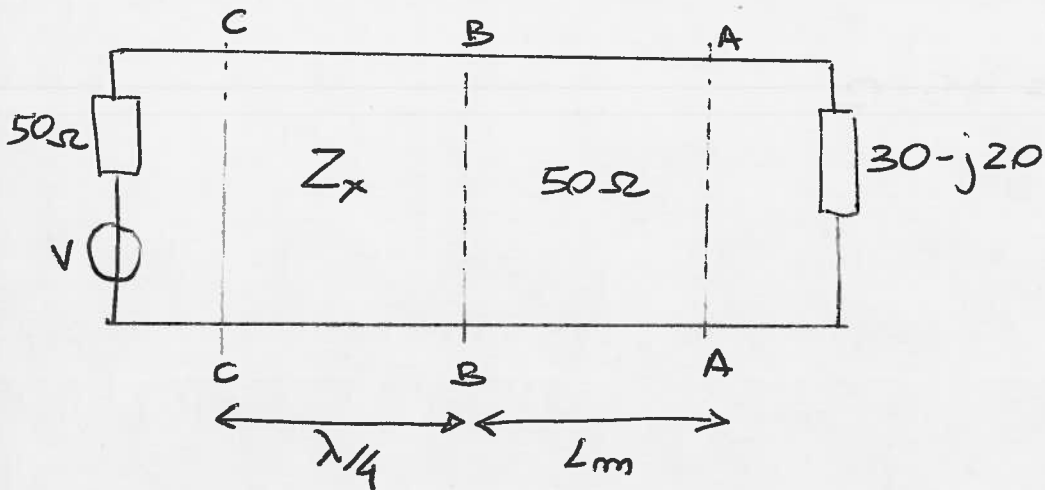EXERCISE

For the transmission line shown in the picture, find the values of Z_x and L_m providing impedance matching at the generator section ($f = 1 \text{ GHz}$, $\lambda = 30 \text{ cm}$)



The transmission line section Z_x can provide impedance matching only if the impedance of the line at section B is real.

The normalized impedance at section A is

$$\bar{z}_{AA} = \frac{Z_{AA}}{50 \Omega} = 0,6 - j0,4$$

In order to have a real impedance at section B the length L_m must be responsible for a rotation around the origin of the Smith Chart up to a crossing with the real axis -

A rotation to the point $\bar{z}_{BB} = 0,49$ is obtained

when $L_m = 0,082 \lambda = 2,46 \text{ cm}$


The impedance Z_{BB} is equal to

$$Z_{BB} = \bar{\epsilon}_{BB} \cdot 50 \Omega = 24.5 \Omega$$

The required characteristic impedance Z_x for the $\lambda/4$ matching section is


$$Z_x = \sqrt{50 \cdot Z_{BB}} = 35 \Omega$$

Smith Chart

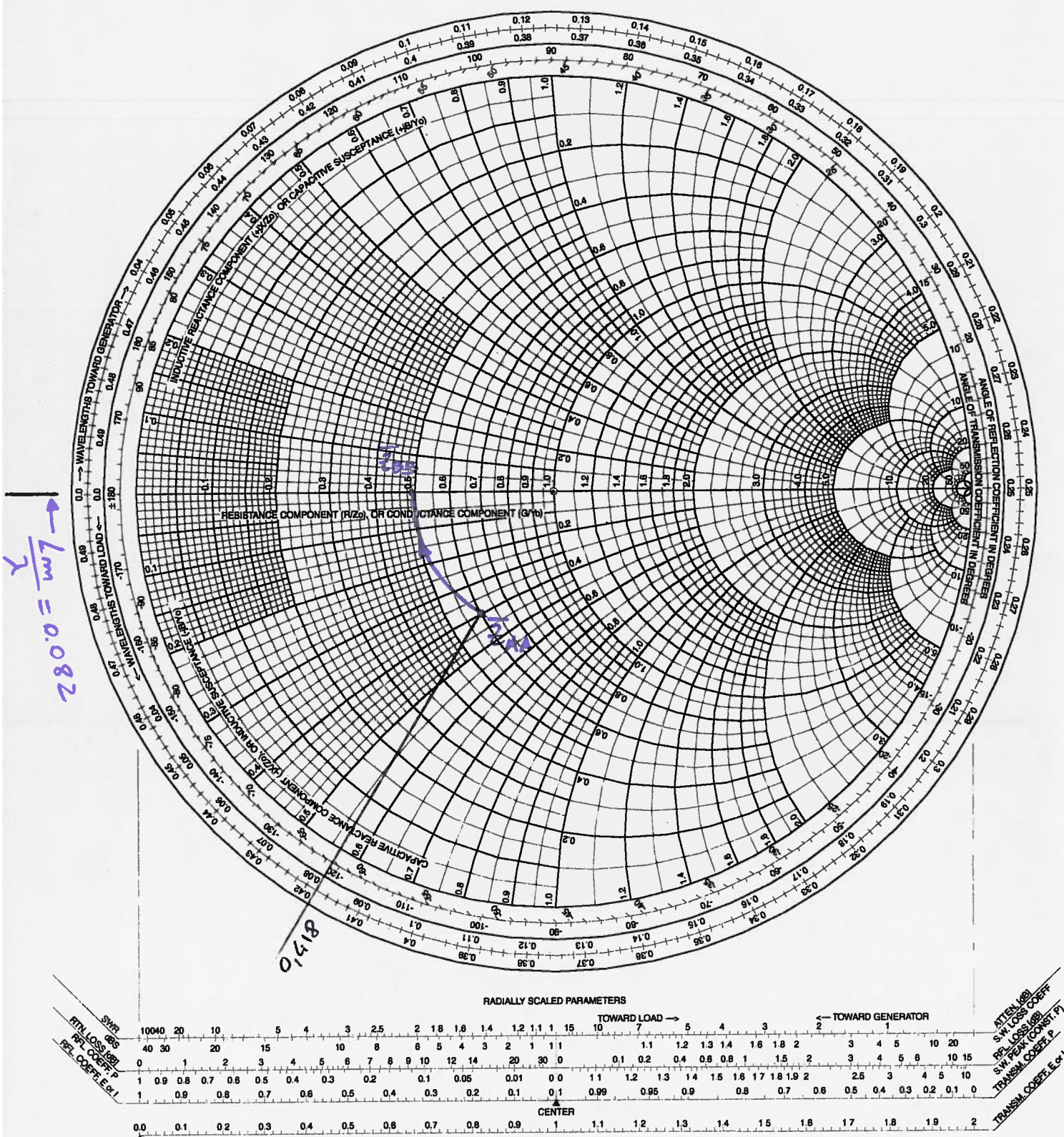

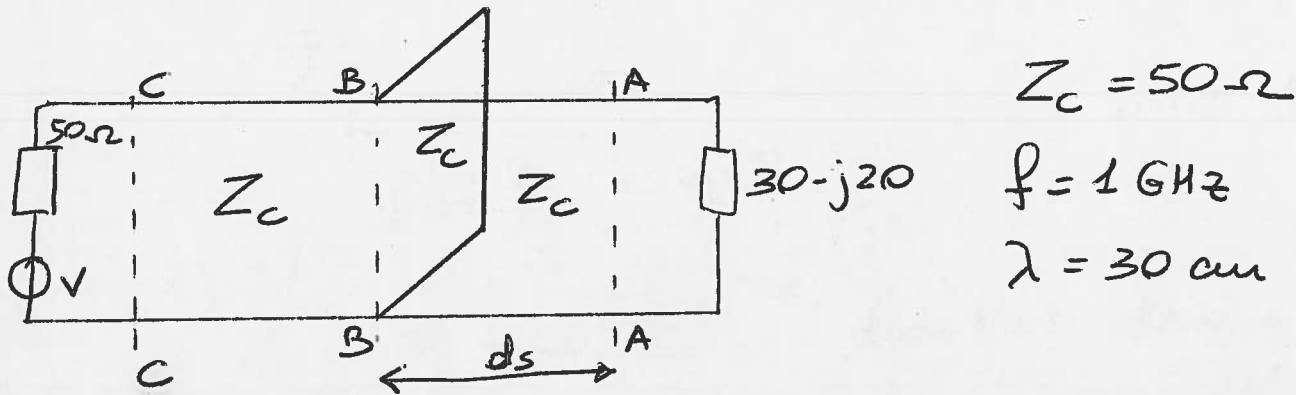EXERCISE (Impedance matching with stub line)

Calculate the length of the lines d_s and l_s in order to have perfect impedance matching at the generator section for the line shown in the picture.



To design an impedance matching stub line in parallel to the main line, it is convenient to work with the Smith chart for admittance

The normalized admittance at section A is

$$\bar{y}_{AA} = \frac{Y_{AA}}{Y_c} = \frac{Z_c}{Z_{AA}} = \frac{50 \Omega}{30 - j20 \Omega} = 1,15 + j0,73$$

The line section d_s must move the point \bar{y}_{AA} to a point with $\text{Re}\{\bar{y}_{BB}\} = 1$

Rotating \bar{y}_{AA} around the center of the Smith chart, the first solution we find is

$$\bar{y}_{BB} = 1 - j0,73$$


The length d_s is given by $\frac{d_s}{\lambda} = 0,348 - 0,168 = 0,18$

$$d_s = 0,18 \lambda = 5,4 \text{ cm}$$

The stub line must add an admittance $\bar{y}_s = +j0,23$ in order to cancel out the imaginary part of \bar{Y}_{in}


By using an open circuit stub

$$d_s = 0,1 \lambda = 3 \text{ cm}$$

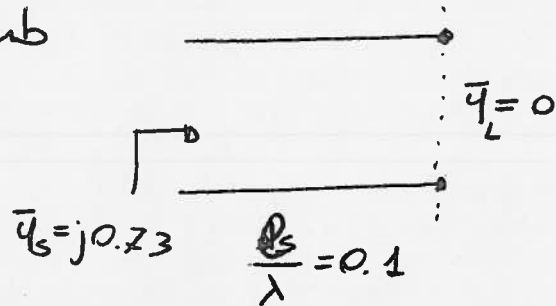


By using a short circuit stub

$$d_s = 0,35 \lambda = 10,5 \text{ cm}$$

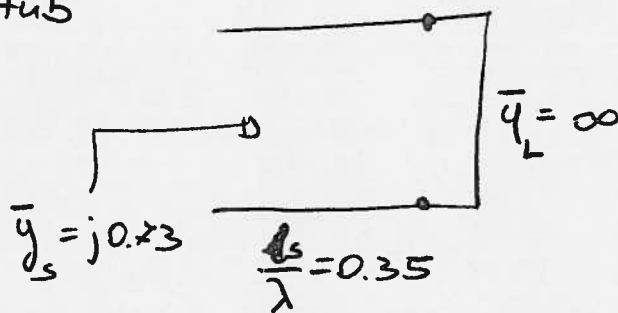

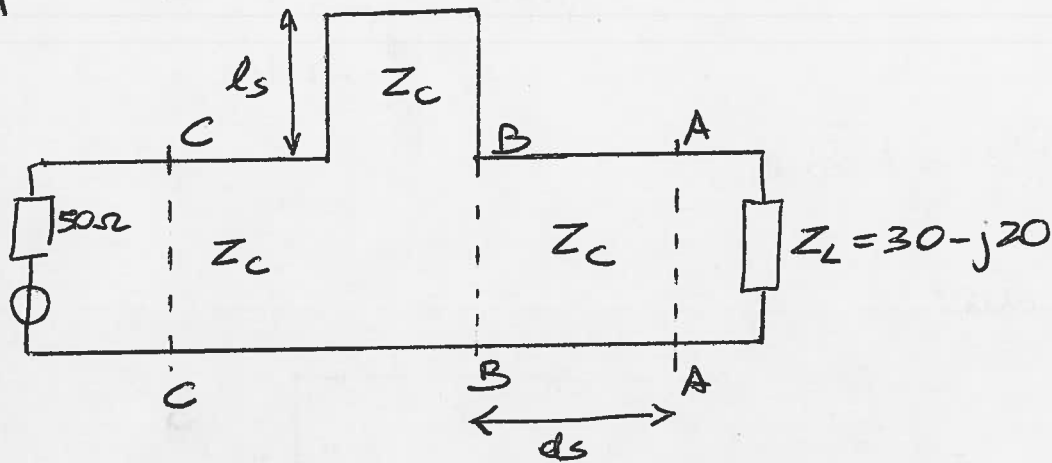EXERCISE (Impedance matching with stub lines)

Calculate the length of the lines d_s and l_s in order to have perfect impedance matching at the generator section for the transmission line shown in the picture



$$f = 1 \text{ GHz}$$

$$\lambda = 30 \text{ cm}$$

The normalized impedance at section A is

$$\bar{z}_{AA} = \frac{Z_L}{Z_c} = 0,6 - j0,4$$

The line section d_s must move the point \bar{z}_{AA} to a point with $\text{Re}\{\bar{z}_{BB}\} = 1$. Rotating \bar{z}_{AA} around the center of the Smith chart, the first solution is

$$\bar{z}_{BB} = 1 + 0,75j$$


The length d_s is given by

$$\frac{d_s}{\lambda} = 0,154 + 0,082 = 0,236 \quad \Rightarrow \quad d_s = 0,236\lambda = 7,08 \text{ cm}$$

The stub line must add an impedance $\bar{z}_{S} = -j0.75$ in order to cancel out the imaginary part of \bar{z}_{BB}


By using an open circuit stub
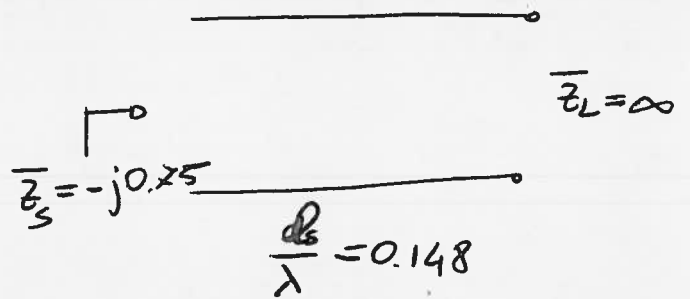
$$l_s = 0.148 \lambda = 4.44 \text{ cm}$$



By using a short circuit stub
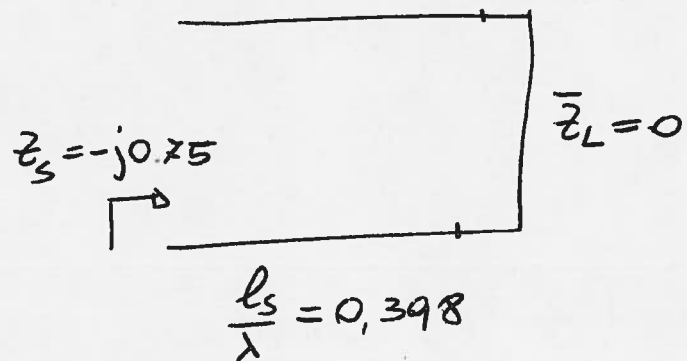
$$l_s = 0.398 \lambda = 11.94 \text{ cm}$$



open circuit stub $\rightarrow l_s = 0.148\lambda$

short circuit stub $\rightarrow l_s = 0.398\lambda$

Smith Chart

